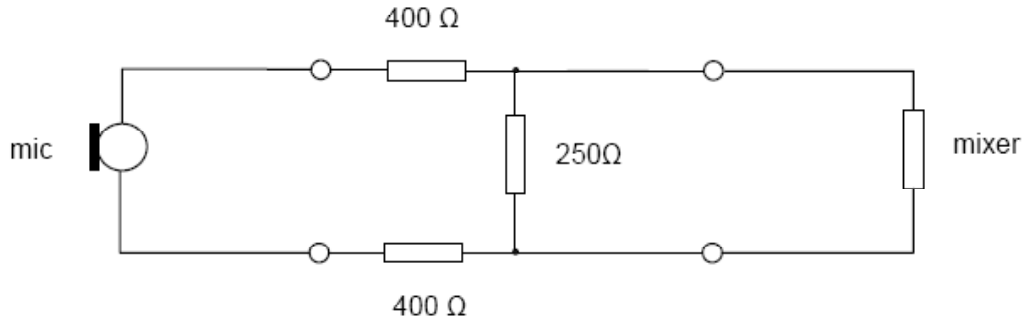


Microphone Pad / Attenuator

Often needed to connect radiomic receiver to over sensitive amplifier inputs



14db balanced mic attenuator (pad)

For unbalanced replace 400 ohm R in signal line with 800 ohm and do not use R in earth / ground line
For normal use nearest preferred R values